

B.Tech. SEM-IV E & TC 2014 Course (CBCS) : SUMMER - 2019
SUBJECT: LINEAR INTEGRATED CIRCUITS

Day : Thursday
 Date: 23/05/2019

Time: 10.00 AM TO 01.00 PM
 Max. Marks: 60

S-2019-2635

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw the diagrams wherever necessary.
- 4) Assume suitable data, if necessary.

- Q.1**
- a) What do you mean by offset voltage? How to compensate offset voltage? (06)
 - b) The 741 C is used as inverting amplifier with a gain of 50. The sinusoidal input voltage has a variable frequency and max. amplitude of 20 mV peak. What is the maximum frequency of input at which output will be undistorted? Assume that amplifier is initially nulled. (04)
- OR**
- a) Define – i) CMRR ii) input offset current iii) input bias current. (06)
 - b) Draw and explain block diagram of IC 741C. (04)
- Q.2**
- a) Design a summing amplifier to add 3 DC input voltage. (06)
 - b) Determine output voltage for open loop differential amplifier with first input voltage = 10 mV (RMS), second input voltage = 20 mV (RMS). Draw output waveforms.
- OR**
- a) Explain use of Op-Amp as differentiator. Draw diagram and derive necessary equation. (06)
 - b) Instrumentation amplifier uses a strain gauge and has following specifications. Unstrained resistance of each of 4 elements of strain gauge is 120Ω , $V_{dc} = 5V$ and Op-Amp supply voltage = $\pm 10V$, $R_1 = 100\Omega$, $R_f = 47K\Omega$. Determine output voltage If change in resistance of each strain gauge element is 0.1Ω . (04)
- Q.3**
- a) For Schmitt trigger, $R_1 = 150\Omega$, $R_2 = 68k\Omega$, $V_{in} = 500mV_{pp}$ sine wave and saturation Voltage = $\pm 14V$. Determine threshold voltage and hysteresis voltage. Also draw the output waveform. (06)
 - b) Derive the equations for output voltage of log amplifier. (04)
- OR**
- a) Draw and explain circuit and waveforms of precision rectifier. (06)
 - b) Write a short note on Hysteresis. (04)
- Q.4**
- a) Design a first order wide band pass filter with $f_L = 400Hz$ and $f_H = 2kHz$. And pass band gain = 4. (06)
 - b) What are advantages of active filters over passive ones? What is butterworth response? (04)
- OR**
- a) Design second order high pass filter having cutoff frequency 2kHz. (06)
 - b) Draw and explains square wave generator. (04)
- Q.5**
- a) Draw and explain block diagram of 555 timers. (06)
 - b) What is the role of low pass filter and VCO in PLL? (04)
- OR**
- a) Design astable multivibrator using 555 having output frequency of 10kHz with 25% duty cycle. (06)
 - b) List application of PLL. Explain any one application of PLL. (04)
- Q.6**
- a) Explain construction and working of V to I convertor. (06)
 - b) Explain construction and working of D to A convertor using R-2R ladder. (04)
- OR**
- a) Explain construction and working of A to D convertor using successive approximation. (06)
 - b) Explain construction and working of I to V convertor. (04)