

BACHELOR OF TECHNOLOGY (CBCS - 2023)
B. Tech. Sem-II Computer Science & Engineering AI & ML : SUMMER : 2025
SUBJECT: DIGITAL ELECTRONICS

Day : Wednesday
Date : 28/05/2025

S-27702-2025

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.
- 4) Draw neat labeled diagrams **WHEREVER** necessary.

- Q.1** Perform the following operation. (10)
- a) Add 10111 and 1001
 - b) Subtract 1000 from 1110
 - c) Multiply 11101 by 101
 - d) Divide 11110 by 101
 - e) Subtract 1011 from 1111

OR

- Q.1** Why are NAND and NOR gates called Universal gates? Derive AND and OR gates using NAND and NOR gates. (10)

- Q.2** Simplify the following expression using Quine Mc Clusky method and realize it using basic gates. (10)
 $F(A,B,C,D) = \sum m(0,1,3,7,8,9,11,15)$

OR

- Q.2** a) Expand $A(\bar{A}+B)(\bar{A}+B+\bar{C})$ TO Maxterms. (05)
b) Expand $A+BC+AB\bar{D}+ABCD$ to minterms. (05)

- Q.3** a) Draw a logic diagram, block diagram, and write a truth table for:
a) Half Adder
b) Half Subtractor (10)

OR

- Q.3** Describe the function of parity bit generators and checkers for even and odd with the help of logic diagram. (10)

- Q.4** Describe the working of T-flip flop and SR-flip flop with the help of truth table. (10)

OR

- Q.4** Design and explain 4-bit PISO shift register in detail. (10)

- Q.5** Draw a state diagram of S-R, J-K, T and D flip flop. List the rules for state assignment. (10)

OR

- Q.5** Explain the following state machines in detail with the help of diagram. (10)
a) Moore state machine
b) Mealy state machine

- Q.6** Describe EEPROM and ROM with its advantages and disadvantages. (10)

OR

- Q.6** Give the logic implementation of (10)
a) 32 X 4-bit ROM using a decoder of suitable size.
b) 8 X 4-bit ROM using a decoder of suitable size.
