

BACHELOR OF TECHNOLOGY (CBCS - 2023)
B. Tech. Sem-II Computer Science & Engineering AI & ML : WINTER: 2025
SUBJECT: DIGITAL ELECTRONICS

Day : Wednesday
Date : 26/11/2025

W-27702-2025

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.
- 4) Draw neat diagrams **WHEREVER** necessary.

Q.1 Perform the following conversions:

- a) (110101.110010) Binary to Octal (02)
- b) (bDF.3E) HEX to Octal (02)
- c) (305.15) Decimal to Binary (02)
- d) (1010011) Gray to Binary (02)
- e) (4136.14) Octal to Decimal (02)

OR

Q.1 Realize the following function using universal logic gates.

- a) X-OR (05)
- b) X-NOR (05)

Q.2 Simplify the following expression using Quine Mc Clusky method and realize it using basic gates. (10)

$$F(A,B,C,D)=\sum m(0,1,2,7,8,9,10,11,14,15)$$

OR

Q.2 State and prove De Morgan's Theorems. (10)
Reduce the expression $\sum m(0,2,3,4,5,6)$ using mapping and implement in NAND logic.

Q.3 Compare Demultiplexer with Decoder. Describe working of 3:8 decoder with neat block diagram and truth table. (10)

OR

Q.3 Draw a logic diagram, block diagram, and write a k-map simplification from truth table for full Adder. (10)

Q.4 Design a synchronous Mod-6 counter using J-K flip flops. (10)

OR

Q.4 Perform the following conversions of flip flops:

- a) SR-flip flop to JK- flip flop (05)
- b) JK flip flop to D-flip flop (05)

(PTO)

Q.5 Design a logic diagram to detect the sequence 1010. (10)

OR

Q.5 Draw state diagram of S-R, J-K, T and D flip flop. List the rules for state assignment. (10)

Q.6 Describe SRAM and DRAM with its advantages and disadvantages. (10)

OR

Q.6 Write a short note on: Programmable Logic Devices. Explain any one PLD in detail. (10)

261125-m-coe-mumbai