

BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)
B. Tech. Sem - I CS&BS : WINTER : 2023
SUBJECT : PRINCIPLES OF ELECTRICAL ENGINEERING

Day : Wednesday

Time : 10:00 AM-01:00 PM

Date : 6/12/2023

W-24132-2023

Max. Marks : 60

N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labelled diagrams **WHEREVER** necessary.
- 4) Use of non-programmable calculator is **ALLOWED**.
- 5) Assume suitable data, if necessary.


Q. 1 Define and write down the units of :

(10)

- | | |
|-------------|-----------|
| i) EMF | iv) Power |
| ii) Current | v) Work |
| iii) Energy | |


OR

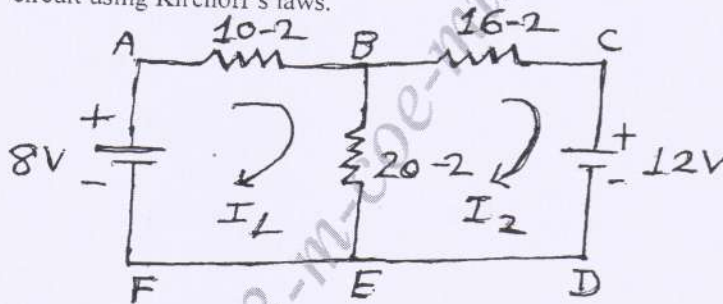State and explain Kirchoff's current law. Find currents I_1 and I_2 for given circuit using Kirchoff's laws. (10)



Q. 2 a) State and explain maximum power transfer theorem. (05)

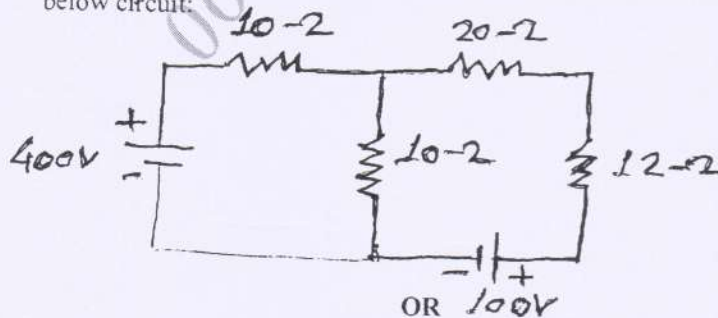b) Apply Thevenin's theorem to calculate the current in $12\ \Omega$ resistance for below circuit: (05)



Derive the equations for delta to star and star to delta conversion for resistive circuit. (10)

Q. 3 Sketch A.C. waveform and power triangle. Define the following parameters related to A.C. system: (10)

- | | |
|-----------------|-----------------|
| i) Cycle | iv) Conductance |
| ii) Frequency | v) Form factor |
| iii) Admittance | vi) Peak factor |

P. T. O.

OR

Sketch and explain R-L-C series circuit. Discuss the concept of resonance (10)
in case of series R-L-C circuit. Derive the formula for resonance frequency.

Q. 4 a) Define the following parameters: (05)

- | | |
|-----------------------------|---------------------------|
| i) Electrostatic field | iv) Absolute permittivity |
| ii) Electric field strength | v) Relative permittivity |
| iii) Permittivity | |

b) Two capacitors $4\mu F$, $8\mu F$ are connected in a) Parallel and b) Series (05)
across a 100 V DC source. Determine following parameters for both
connections:

- Energy stored in each capacitor.
- Equivalent capacitance of that combination.

OR

Define battery and list out its different types. Explain construction and (10)
working of Nickel - Cadmium battery in detail and also write down different
applications of Nickel - Cadmium battery.

Q. 5 a) Define the following terms: (05)

- | | |
|-----------------------------|-----------------------------|
| i) Magnetic field | iv) Magnetic field strength |
| ii) Magnetic flux | v) Reluctance |
| iii) Magnetic field density | |

b) State and explain Faraday's law of Electromagnetic Induction. (05)

OR

Define efficiency and voltage regulation related to performance of single (10)
phase transformer. Explain direct load test on single phase transformer to
determine efficiency and regulation.

Q. 6 a) Write down the different types of wiring and list out different safety devices (05)
used in electrical system.

b) Discuss the importance of electrical earthing in short and list out different (05)
safety devices used in electrical system.

OR

What are the different types of lamps used in illumination system? Explain (10)
construction and working of fluorescent tube in detail with neat diagram.

* * * * *