

B.Tech. SEM -IV Info. Tech. 2014 Course (CBCS) : SUMMER - 2019
SUBJECT: DIGITAL ELECTRONICS AND LOGIC DESIGN

Day: Tuesday
Date: 28/05/2019

Time: 10.00 AM TO 01.00 PM
Max Marks: 60

S-2019-2619

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw diagrams **WHEREVER** necessary.

-
- | | | |
|-----------|---|------|
| Q.1 | List and explain characteristics of digital IC's. | (10) |
| OR | | |
| Q.1 | Compare and discuss characteristics of TTL and CMOS. | (10) |
| Q.2 | Simplify using Quine McCluskey method
$F = \sum (0,1,2,3,5,7,8,9,11,14)$ | (10) |
| OR | | |
| Q.2 | Explain k map representation of logic functions with suitable example. | (10) |
| Q.3 | Explain 3-bit ripple or asynchronous counter in detail. | (10) |
| OR | | |
| Q.3 | Explain D and T flip flops in detail. | (10) |
| Q.4 | Explain Moore machine representation. | (10) |
| OR | | |
| Q.4 | Draw state diagram of different flip flops. | (10) |
| Q.5 | Explain content addressable memory with suitable example. | (10) |
| OR | | |
| Q.5 | Describe DDR and QDR SRAM with its advantages and disadvantages. | (10) |
| Q.6 | Demonstrate design of simple controller. | (10) |
| OR | | |
| Q.6 | Discuss VHDL modeling styles. | (10) |