

**BACHELOR OF TECHNOLOGY (C.B.C.S.) (2021-COURSE)**  
**B. Tech. Sem - I Electrical & Computer Engineering : WINTER- 2022**  
**SUBJECT : ELECTROMAGNETICS & ITS APPLICATIONS**

Day : Friday

Time : 10:00 AM-01:00 PM

Date : 13-01-2023

W-25145-2022

Max. Marks : 60

**N.B.**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.
- 4) Draw neat labeled diagrams **WHEREVER** necessary.

- Q.1 a) Explain the concept of Active and Passive elements. (05)  
b) Explain the concept of Voltage and current sources. (05)

**OR**

- Q.1 a) Describe with diagram super node and super mesh analysis. (05)  
b) Write short note on network reduction using series parallel and star delta transformations. (05)

- Q.2 a) Explain the concept of flux, flux density, field strength. (05)  
b) Compare electric and magnetic circuits. (05)

**OR**

- Q.2 a) Describe Faradays law of electromagnetic induction. (05)  
b) State the concept of statically and dynamically induced emf. (05)

- Q.3 a) Explain the following : sinusoidal, square and triangular wave form. (05)  
b) Write short note on analysis of series circuits. (05)

**OR**

- Q.3 a) Three circuits in parallel take the following currents : (05)

$$i_1 = 20 \sin 314 t, i_2 = 30 \sin \left( 314 t - \frac{\pi}{4} \right), i_3 = 40 \cos \left( 314 t + \frac{\pi}{6} \right).$$

Find

- i) the expression for the resultant current and
- ii) its rms value and frequency.

If the circuit has a resistance of  $2 \Omega$ , what is the energy loss in 10 hours?

- b) A 230 v, 50 Hz AC supply is applied to a coil of 0.06 H inductance and  $2.5 \Omega$  resistances connected in series with a  $6.8 \mu F$  capacitor. Draw the circuit diagram for above values. Calculate i) impedance ii) current iii) phase angle between current and voltage iv) power factor & v) power consumed. (05)

- Q.4 a) Explain the necessity of three phase system. (05)  
b) Explain the meaning of phase sequence. (05)

**OR**

- Q.4 a) Phase voltage and current of a star-connected inductive load is 150V and 25 A. Power factor of load is 0.707 (lag). Assuming that the system is 3-wire and power is measured using two watt meters, find the reading of watt meters. (05)  
b) Write short note on balanced supply and balanced load. (05)

PTO

- Q.5 a) Explain the construction and principle of operation of single phase transformer. (05)  
b) Describe the equivalent circuit and phasor diagram of single phase transformer. (05)

OR

- Q.5 a) The maximum flux density in the core of a 250/3000 volts, 50 Hz single phase transformer is  $1.2 \text{ Wb/m}^2$ . If the cmf per turn is 8 volt, determine i) primary and secondary turns & ii) area of the core. (05)  
b) Describe losses in transformer. (05)
- Q.6 a) Write short note on transformer on no-load and on load. (05)  
b) Write short note on efficiency of transformer, condition of maximum efficiency, all day efficiency. (05)

OR

- Q.6 a) In a no-load test of single phase transformer, the following test data were obtained :  
Primary voltage : 220V  
Secondary voltage : 110V  
Primary current : 0.5A  
Power input : 30W  
Find the following : i) the turn ratio ii) the magnetizing component of no-load current, iii) its working (or loss) component & iv) the iron loss. The resistance of the primary winding =  $0.6 \Omega$ . (05)  
b) Write short note on regulation of a transformer. (05)

\*\*\*\*\*