

B.Tech. sem-III E & TC

B. Tech. Sem -III (E & TC Engg.) (2014 COURSE) (CBCS) :
SUMMER - 2019

SUBJECT : NETWORK THEORY

Day : Wednesday
Date : 15/05/2019


Time : 02.30 PM TO 05.30 PM
Max. Marks : 60

S-2019-2590


N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labeled diagram **WHEREVER** necessary.
- 4) Use of non-programmable calculator is **ALLOWED**.
- 5) Assume suitable data, if necessary.

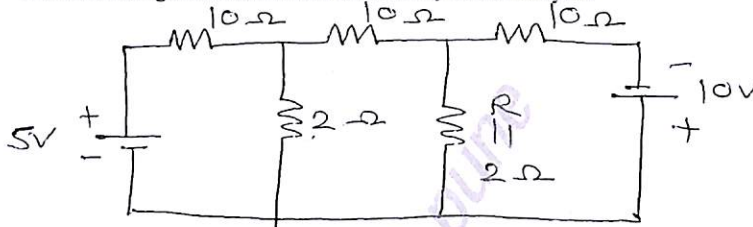
Q. 1 a) Find the voltage across R in the network by mesh analysis: (05)



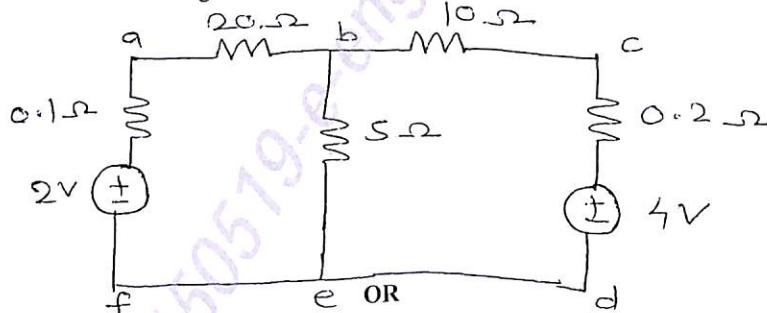
b) Find current through branch b-e using Norton theorem: (05)



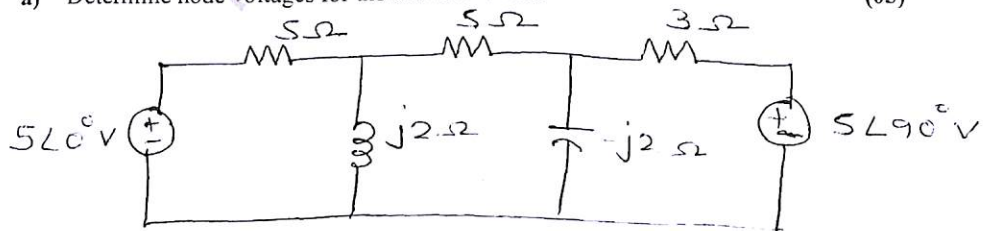a) Determine node voltages for the shown network: (05)



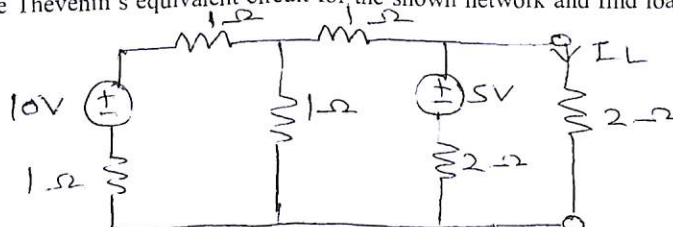b) Draw the Thevenin's equivalent circuit for the shown network and find load current: (05)



P. T. O.

Q. 2 a) What is tree and what are the properties of tree? (05)


b) Draw the oriented graph from reduced incidence matrix: (05)

$$A = \begin{bmatrix} 0 & 0 & -1 & 1 & -1 & 0 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 1 & -1 \end{bmatrix}$$


OR

a) What is the use of network equilibrium equation? (05)

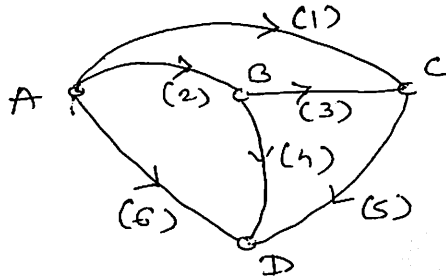b) Find the proper cut-sets for the following graph: (05)



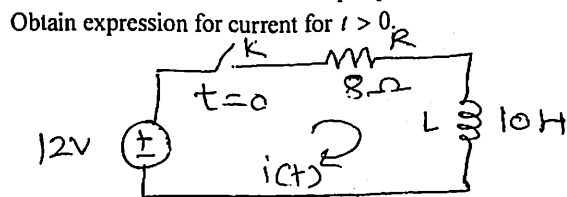Q. 3 a) In the circuit shown switch is kept open for long time. At $t = 0$ it is closed. (05)



b) For series RL circuit (05)

Find: i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$ Where $V = 200V$, $R = 5\Omega$ and $L = 3H$

OR

a) Find transient response of driven R-C circuit (05)

b) What are the initial conditions of passive components? (05)

Q. 4 a) Find effect of anti-resonance on selectivity and bandwidth. (04)

b) A practical parallel resonant circuit consists a coil of 0.1 H inductance with 10 Ω leakage resistance with a 10 μF capacitor in parallel with it. Find frequency at which current in the circuit which is properly resistive. Also find impedance under resonance. (06)


OR

a) A series resonant circuit has impedance of 500 Ω at resonant frequency, cut-off frequencies are 10 KHz and 100 KHz. Determine: (07)

- i) Resonant frequency
- ii) Value of R, L, C components
- iii) Quality factor at resonant frequency

b) What is anti-resonance and what is the application of the same? (03)

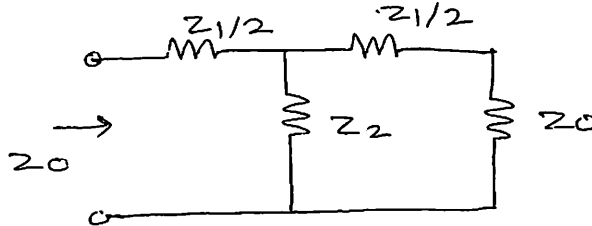Q. 5 a) Derive Z_o for given network: (05)




b) A π - Low pass filter network consists of a series arm inductance of 20 mH and two shunt arm capacitor of 0.16 μ F each. Calculate cut-off frequency, attenuation and phase shift at 1.5 KHz. (05)

OR

a) What are the design formulae of K-high pass filter? (05)

b) Design k-T section LPF to be terminated into $1k\Omega$ and having a cut-off frequency of 3 KHz. Determine frequency at which filter offers an attenuation of 20dB. (05)

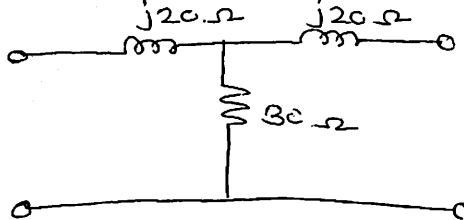Q. 6 a) For the network shown determine Z and Y parameter. (05)



b) Derive Z parameter in terms of ABCD parameter. (05)

OR

a) Find symmetry and reciprocity conditions of h parameters. (05)

b) When two networks are connected in parallel find y parameters for the combined network. (05)