

B.Tech. SEM -I ( Civil/ Electrical/ Mechanical/ Production/ Computer/  
 Info. Tech. 2014 Course (CBCS) : WINTER - 2018  
 SUBJECT: FUNDAMENTALS OF ELECTRICAL ENGINEERING

Day : Saturday  
 Date: 01/12/2018

W-2018-2266

Time : 10.00 AM TO 01.00 PM  
 Max. Marks : 60

N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labeled diagram **WHEREVER** necessary.
- 4) Assume suitable data, if necessary.

Q. 1 a) Prove that: (05)


$$\alpha_t = \frac{\alpha_0}{1 + \alpha_0 t}$$

- b) A belt driven pulley 0.4 m in diameter rotates at a speed of 4 rps. The tension in the tight side of belt is 450 N and that on slack side is 100 N. Calculate: (05)
- i) Torque on the pulley
  - ii) The power developed


OR

- a) Define temperature coefficient of resistance. Also derive an expression of it. (05)
- b) A specimen of copper wire has a temperature coefficient of  $\frac{1}{254.5}$  per  $^{\circ}\text{C}$  at  $20^{\circ}\text{C}$ . Find the temperature coefficient at  $0^{\circ}\text{C}$ . (05)

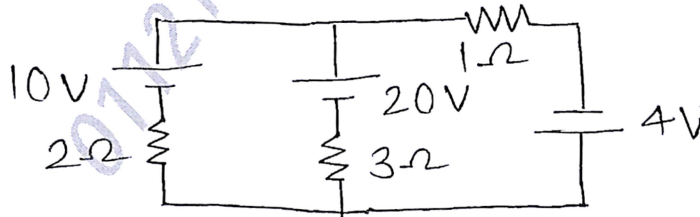
Q. 2 a) Calculate current in  $3\ \Omega$  resistor using Thevenin's theorem: (05)



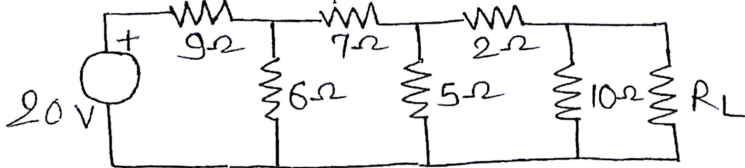b) Determine  $R_L$  for maximum power transfer: (05)




a) Find  $R_{AB}$  (05)

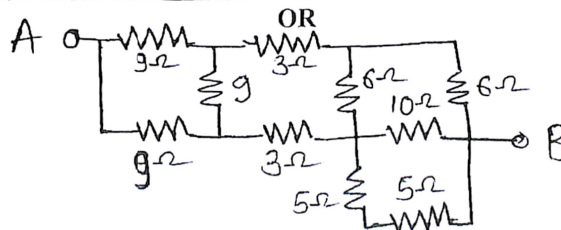

P. T. O.

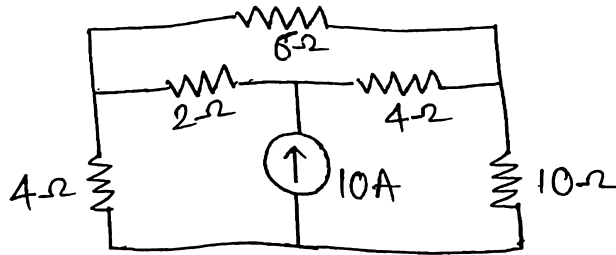- b) Find the voltage drop in  $10\ \Omega$  resistor using Nodal analysis: (05)



- Q.3 a) Define the following. Give their expression and units: (05)
- Electric flux density
  - Permittivity

- b) Calculate the capacitance of a parallel plate capacitor consisting of two metal plates each  $60\text{ cm} \times 60\text{ cm}$  separated by a dielectric  $1.5\text{ mm}$  thick and of relative permittivity  $3.5$ . If a potential of  $500\text{ V}$  is applied find charge, electric flux density (05)

OR

- a) Derive the expression for the energy stored in capacitor. (05)
- b) A parallel plate capacitor has two metal plates of area  $2.5\text{ m}^2$  separated by three slabs of different dielectric materials. The relative permittivity of these dielectric materials are  $1, 3, 5$  and the thickness is  $0.5, 1, 2\text{ mm}$ . respectively. Calculate: Capacitance of the capacitor. (05)

- Q.4 a) Explain in brief (05)
- Statically induced EMF
  - Dynamically induced EMF

- b) A  $3300/110\text{ V}, 50\text{ Hz}, 50\text{ kVA}$  transformer has full load copper loss of  $1600\text{ W}$  and iron loss of  $1800\text{ W}$ . Estimate transformer efficiency at: (05)
- Full load and  $0.7$  lagging p.f
  - Half load and  $0.85$  lagging p.f

OR

- a) Write a short note on B-H curve. (05)
- b) Draw the neat connection diagram and explain the procedure for determining voltage regulation and efficiency by direct loading method for transformer having ratings  $1\text{ kVA}, 230/115\text{ V}, 1\text{ phase}, 50\text{ Hz}$ . Also write proper ranges of meters used. (05)

- Q.5 a) What is series resonance? Obtain the expression for resonant frequency. (05)
- b) Define the following in case of an AC quantity:  
Average value, RMS value, instantaneous value, form factor, peak factor

OR

- a) Define: (05)
- Impedance
  - Admittance of circuit and sketch impedance and admittance triangle.

- b) A circuit consisting of resistance of  $20 \Omega$  and inductance of  $0.1 \text{ H}$  in series, is connected across single phase  $220 \text{ V}$ ,  $50 \text{ Hz}$  supply: (05)

Calculate:

- i) Current drawn
- ii) P.f.
- iii) Power consumed by circuit

- Q. 6 a) Why earthing is necessary? Write a brief note on any one type of earthing with sketch. (05)

- b) Write a detailed note on LED. (05)

OR

- a) State and explain various charges included in electricity bill. (05)

- b) State various types of electric wiring. Explain any one. (05)

\* \* \* \* \*

---