

BACHELOR OF TECHNOLOGY (CBCS - 2023)
B. Tech. Sem-I INFORMATION TECHNOLOGY : SUMMER : 2024
SUBJECT: DIGITAL ELECTRONICS

Day : Tuesday
Date : 14/05/2024

S-27658-2024

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.

-
- Q.1 Illustrate the all numbering systems (Binary,hex.octal,Decimal). (10)
- OR
- Q.1 Apply the knowledge of code converter Binary to BCD. (10)
- Q.2 Describe the all logic gates along with example. (10)
- OR
- Q.2 Minimize the following expression using K-map and implements using logic gates (10)
 $Y = \sum(4, 5, 6, 7, 12, 13, 14, 15)$
- Q.3 Explain Full adder with suitable diagram. (10)
- OR
- Q.3 Design 16:1 multiplexer with suitable diagram. (10)
- Q.4 Describe JK and T flip flop in detail. (10)
- OR
- Q.4 Explain SISO and PISO shift register. (10)
- Q.5 Differentiate Melay machine and Moore machine. (10)
- OR
- Q.5 Describe ASM chart notation in detail. (10)
- Q.6 Explain types of Memories (10)
- OR
- Q.6 Explain the architecture of PLA and PLD. (10)

* * * * *