

**BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)**  
**B. Tech. Sem - I Computer Science & Engineering : WINTER : 2024**  
**SUBJECT: DIGITAL ELECTRONICS**

Day : Friday  
Date : 06/12/2024

W-24021-2024

Time : 10:00 AM-01:00 PM  
Max. Marks : 60

**N.B.**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.
- 4) Draw neat labeled diagrams **WHEREVER** necessary.

- Q.1** Perform the following conversions **(10)**
- a)  $(10101101.0111)_2 = ( )_8$
  - b)  $(615.25)_8 = ( )_{16}$
  - c)  $(BC66.AF)_{16} = ( )_8$
  - d)  $(12.125)_{10} = ( )_2$
  - e)  $(A3E)_{16} = ( )_{10}$

**OR**

- Q.1** Describe different types of Digital codes and state their application. **(10)**

- Q.2** State different Boolean Laws. **(10)**  
Simplify following expression using Boolean Laws and implement using logic gates.

- i)  $Y = (AB + BC).C$
- ii)  $Y = ABC + \bar{A} + \bar{A}BC$

**OR**

- Q.2** Simplify following expressions using tabulation method (Quine McCluskey) and implement using logic gates. **(10)**  
 $F(A,B,C,D) = \sum m(0, 2, 3, 6, 7, 8, 10, 13)$

- Q.3** Design 4 bit Gray to Binary code converter. **(10)**

**OR**

- Q.3** Describe working of 8:1 Multiplexer with suitable circuit diagram and truth table. **(10)**

- Q.4** Design 3 bit synchronous up counter and draw neat timing diagram. **(10)**

**OR**

- Q.4** Describe different types of flip-flops with truth tables and circuit diagrams. **(10)**

- Q.5** Describe notation of ASM chart. Draw ASM chart and state diagram. **(10)**

**OR**

- Q.5** Design a sequence detector to detect sequence 1 1 0 1. **(10)**

- Q.6** Describe architecture of PLA with neat block diagram and explain with suitable example. **(10)**

**OR**

- Q.6** Explain in detail semiconductor memories. **(10)**

\*\*\*\*\*