

BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)
B. Tech. Sem - I Computer Science & Engineering : WINTER: 2025
SUBJECT: DIGITAL ELECTRONICS

Day : Friday
Date : 12/12/2025

W-24021-2025

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.
- 4) Draw neat labeled diagrams **WHEREVER** necessary.

- Q.1 Convert the following** (10)
- i) $(101011.101)_2 = (?)_8$
 - ii) $(375.25)_{10} = (?)_2$
 - iii) $(152.25)_8 = (?)_{10}$
 - iv) $(6BA)_{16} = (?)_2$
- OR**
- Q.1 Define universal gates and its types in detail.** (10)
- Q.2 Simplify the following expressions using k-map and implement using logic gates.** (10)
 $f(A, B, C, D) = \sum m (0, 2, 5, 6, 7, 8, 10, 13, 15)$
- OR**
- Q.2 Simplify the following function using Quine Mc Cluskey method and implement using logic gates** (10)
 $f(A, B, C, D) = \sum m (0, 1, 3, 7, 8, 9, 11, 15)$
- Q.3 Describe the working of 3 X 8 decoder with truth table and circuit diagram.** (10)
- OR**
- Q.3 Design 4 bit Binary to Gray code converter.** (10)
- Q.4 Explain in detail J-K flip-flop with neat diagram, excitation table, characteristic table and equation.** (10)
- OR**
- Q.4 Design 4-bit Asynchronous down counter.** (10)
- Q.5 Describe notations of ASM chart. Draw ASM chart and state diagram for 3 bit.** (10)
- OR**
- Q.5 What is a state machine? Explain Moore and Mealy state machine with suitable examples.** (10)
- Q.6 Classify semiconductor memories in detail.** (10)
- OR**
- Q.6 Explain in detail with suitable example architecture of PLA.** (10)
