

BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)
Computer Science & Business Systems
B. Tech. Sem - II :SUMMER : 2023
SUBJECT : PRINCIPLES OF ELECTRONICS ENGINEERING

Day : Thursday

Time : 10:00 AM-01:00 PM

Date : 1/6/2023

S-24140-2023

Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Use of non-programmable calculator is **allowed**.
- 4) Assume suitable data **WHEREVER** necessary.
- 5) Draw neat diagram **WHEREVER** necessary.

Q.1 Draw and explain P-type and N-type Extrinsic semiconductors in detail with diagram. Also define majority and minority carriers in both types of extrinsic semiconductors. (10)

OR

Q.1 Explain conductor, semiconductor and insulator with the help of Energy band diagram. (10)

Q.2 Draw and explain Bridge Rectifier with the help of waveforms. State the advantages of above circuit. (10)


OR

Q.2 What is mean by DC load line and explain Quiescent(Q) point? Draw and explain linear piecewise model for diode. (10)

Q.3 Define the current amplification factor for common emitter configuration, common base configuration and common collector configuration. Derive the relation between them. (10)

OR

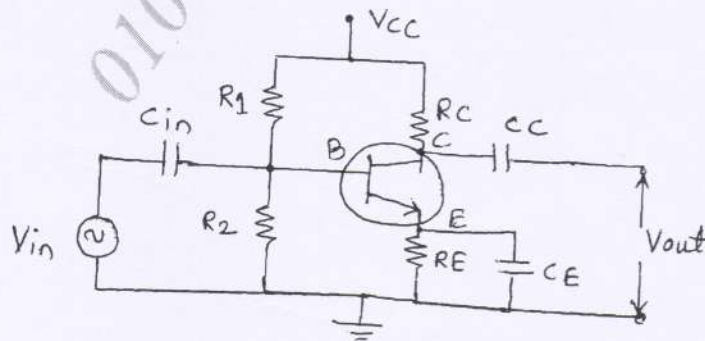Q.3 a) A voltage divider circuit is shown in fig. has values as follows, $I_E = 2\text{mA}$, $I_B = 50\mu\text{A}$, $V_{BE} = 0.2\text{V}$, $R_E = 1\text{K}\Omega$, $R_2 = 10\text{K}\Omega$ and $V_{CC} = 10\text{V}$. Calculate value of R_1 . (06)



b) Describe the Thermal Runaway process with diagram. (04)

Q.4 Describe the construction and operation of n-channel enhancement MOSFET. Also draw drain and transfer characteristics for the same. (10)

OR

Q.4 Explain common source and common gate configuration of MOSFET with circuit diagram. (10)

PTO

Q.5 What is mean by feedback? Explain Inverting and Non-inverting Amplifier with diagram. (10)

OR

Q.5 Draw and explain the operation of Op-Amp as Integrator and Differentiator in detail. (10)

Q.6 Which gates are called as universal gates and why? Explain DeMorgans' first and second theorem with truth table and logic diagram. (10)

OR

Q.6 Define counter. State the types of counter. Draw and explain the operation of 4-bit Johnson counter using D-flip-flop with timing diagram. (10)

010623-m-coe-mumbai