

**BACHELOR OF TECHNOLOGY (CBCS - 2023)**  
**B. Tech. Sem-I Computer Science & Business Systems : WINTER : 2024**  
**SUBJECT: PRINCIPLES OF ELECTRICAL ENGINEERING**

Day : Tuesday  
Date : 10/12/2024

**W-27624-2024**

Time : 10:00 AM-01:00 PM  
Max. Marks : 60


**N.B.**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labelled diagrams **WHEREVER** necessary.
- 4) Use of non - programmable **CALCULATOR** is allowed.
- 5) Assume suitable data if necessary.

- Q.1 a)** Define EMF and resistance. Discuss the factors affecting resistance value. (05)
- b)** Calculate resistance of 50 m length of aluminum wire having uniform cross sectional area of  $0.05 \text{ mm}^2$  and having resistivity of  $50 \mu\Omega\text{-cm}$ . If the wire is drawn four times of it's original length, calculate value of new resistance. (05)

**OR**

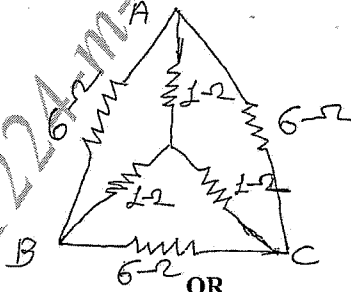- Q.1** State and explain Kirchhoff's laws. Define and write down the unit of following terms: (10)  
i) Work ii) Power iii) Energy
- Q.2** Write down the statement of Superposition theorem and Thevenin's theorem. Calculate the value of resistance  $R_{BC}$  in following circuit by using star/delta transformation. (10)



- Q.2** Write down the statement of Maximum power transfer theorem and Norton's theorem. Derive the condition for maximum power transfer for the resistive circuit. (10)
- Q.3** Sketch and explain power triangle. Elaborate the concept of resonance in series R-L-C circuit. (10)
- OR**
- Q.3** Derive the equations to convert delta connected resistive network into equivalent star connected network. (10)
- Q.4** List out different types of batteries. Explain construction, working principle and applications of lead-acid battery. (10)

**P.T.O.**

OR

Q.4 Derive the expression for equivalent capacitance for following condition: (10)  
i) Capacitors are connected in series.  
ii) Capacitors are connected in parallel.

Q.5 Explain Faradays law of electromagnetic induction and discuss the following (10)  
concepts in short:  
i) Self inductance ii) Mutual inductance iii) Coefficient of coupling

OR

Q.5 Define transformer and discuss in short the following concepts related to (10)  
operation of single phase transformer:  
i) Voltage regulation ii) Efficiency iii) EMF equation iv) Losses in  
transformer

Q.6 List out different types of wiring system and wiring accessories. Explain cleat (10)  
wiring in detail.

OR

Q.6 Discuss necessity of earthing. List out different types of earthing and explain (10)  
rod earthing in detail.

\* \* \*

101224-m-coe-mumbai