

# B.Tech sem-III Electrical

B. Tech. Sem -III (Electrical Engg.) 2014 COURSE (CBCS) :  
SUMMER - 2019

SUBJECT : LINEAR AND DIGITAL INTEGRATED CIRCUITS

Day: Monday  
Date: 13/05/2019

Time: 02.30 PM TO 05.30 PM  
Max. Marks:60

S-2019-2563

**N.B.**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat diagrams **WHEREVER** necessary.

- Q.1** a) Draw neat diagram of instrumentation amplifier. Describe its operation and its applications. (06)
- b) Define slew rate, PSRR. State its typical values. (04)

**OR**

- Q.1** a) Draw circuit diagram of I to V converter and explain its operation (06)
- b) Draw circuit diagram of adder for  $V_1 = +1V$  and  $V_2 = -0.5V$  and find output voltage. (04)

- Q.2** a) Draw circuit diagram of triangular waveform generator and describe its operation with waveforms. (06)

- b) What are clipping and clamping circuits? Describe by suitable waveforms. (04)

**OR**

- Q.2** a) Draw neat diagram of differentiator and describe its operation with waveforms for square wave input. Write mathematical equation. (06)

- b) Draw circuit diagram of zero crossing detector and explain. (04)

- Q.3** Draw pin diagram and block diagram of IC 723. Describe its operation and state its specifications. Define line regulation and load regulation. (10)

**OR**

- Q.3** Draw block diagram of IC 555 as monostable multivibrator. Describe its operation with all waveforms. Write down the equation of time delay provided. (10)

- Q.4** a) Express the number  $(-37)_{10}$  as an 8 bit number in sign magnitude. (02)

- b) Reduce the following Boolean expressions using K- map. (08)

i)  $f(A,B) = \bar{A}B + \bar{A}\bar{B} + AB$

ii)  $f(A,B) = AB + \bar{A}B$

iii)  $f(A,B,C) = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$

iv)  $f(X,Y,Z) = \bar{X}\bar{Y}Z + X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + XY\bar{Z} + \bar{X}YZ$

**OR**

- Q.4** a) Find the sum of the following using 2's complement. (04)

i)  $-1011$  &  $-0101$

ii)  $+0111$  &  $-0011$

- b) List the various laws stated in Boolean Algebra. (06)

P.T.O.

Q.5 a) Explain the function of (n:1) multiplexer with block diagram and truth table. (06)

b) Implement the given function using 8:1 multiplexer (04)  
 $F(A, B, C) = \sum M(0, 2, 3, 5)$

OR

Q.5 a) Implement 1:8 demultiplexer using two 1:4 demultiplexers. (06)

b) Implement the given function using 4:1 multiplexer (04)  
 $f(A, B) = \pi M(1, 3, 4)$

Q.6 a) Design 3 bit asynchronous up counter with the help of JK flip flop and draw its logic diagram. Also show the timing waveforms. (08)

b) Draw the symbol and write truth table of SR & JK flip flop. (02)

OR

Q.6 a) Explain the working of 4 bit twisted ring counter with neat block diagram. (06)

b) What is master -slave JK flip flop? Explain its working with logic diagram & truth table. (04)

\* \* \* \* \*

130579-e-engg-pune