

BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)
B. Tech. Sem - I COMPUTER SCIENCE & BUSINESS SYSTEMS : SUMMER : 2024
SUBJECT: PRINCIPLES OF ELECTRICAL ENGINEERING

Day : Tuesday
Date : 14/05/2024

S-24132-2024

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.


- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.
- 4) Draw neat labeled diagrams **WHEREVER** necessary.
- 5) Use of non-programmable calculator is allowed.

Q.1 State and explain Kirchhoff's laws. Explain concept of ideal current source and practical current source in detail. (10)

OR

Q.1 a) Define resistance and discuss the factors affecting resistance value. (05)

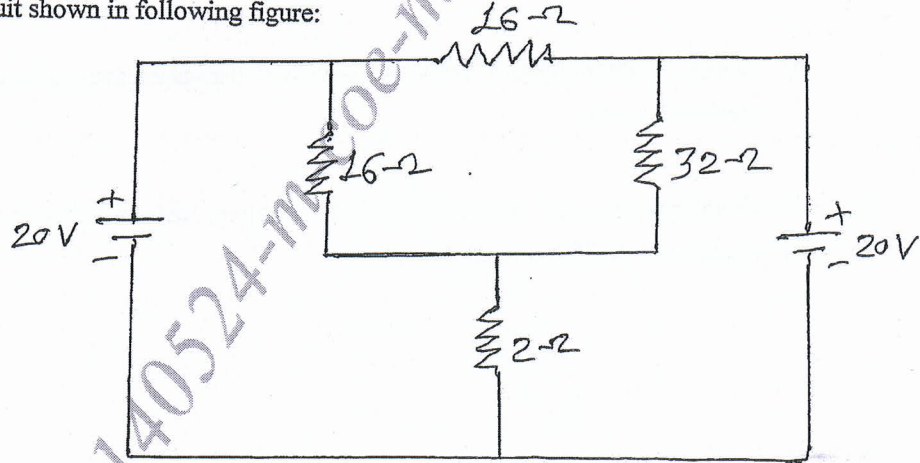b) Using Kirchhoff's laws, calculate the current flowing in $2\ \Omega$ resistance for the circuit shown in following figure: (05)



Q.2 State and explain Thevenin's theorem and Maximum power transfer theorem. (10)
Derive the condition for maximum power transfer for the resistive circuit.

OR

Q.2 Derive the formula for star to delta conversion and delta to star conversion for resistive circuit. (10)

Q.3 Sketch AC waveform and define the following terms related to AC circuit: (10)
i) Cycle ii) Time period iii) Frequency iv) Peak value

OR

Q.3 Sketch power triangle. Explain the concept of resonance in series R-L-C circuit and derive the formula for resonant frequency. (10)

P.T.O.

Q.4 Two condensers of $30 \mu\text{F}$ and $60 \mu\text{F}$ are connected in series across 200 V D.C. (10)
supply. Find i) Equivalent capacitance ii) The charge on each condenser
iii) Potential difference across the condensers.

OR

Q.4 Classify electric batteries. Discuss construction, working and applications of (10)
Nickel- Cadmium cell.

Q.5 State and explain Faraday's law of electromagnetic induction. Compare magnetic (10)
circuit and electric circuit.

OR

Q.5 Derive E.M.F. equation of single-phase transformer and explain direct load test (10)
method to determine efficiency and voltage regulation of single-phase transformer.

Q.6 a) Define transducer and sensor. What are the basic requirements of good quality (05)
transducer?

b) List-out different types of earthing system and discuss necessity of earthing in (05)
electrical system.

OR

Q.6 Sketch and explain basic layout of distribution system. List-out different types of (10)
wiring system and different types of lamps.
