

BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)
B. Tech. Sem - II COMPUTER SCIENCE & ENGINEERING AI & ML : SUMMER : 2024
SUBJECT: DIGITAL ELECTRONICS

Day : Thursday
Date : 30/05/2024

S-23932-2024

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Use of **non-programmable calculator** is allowed.
- 4) Assume suitable data **WHEREVER** necessary.
- 5) Draw neat diagram **WHEREVER** necessary.

Q.1 Why are NAND and NOR gates called Universal gates? Derive AND and OR gates using NAND and NOR gates. (10)

OR

Q.1 Perform the following conversions: (10)

- a) (110111.101010) Binary to Octal
- b) (13.15) Decimal to Binary
- c) (1034.20) Octal to Decimal
- d) (C9D.B4) HEX to Octal
- e) (1011001) Gray to Binary

Q.2 Simplify the following expression using K-map and realize it in universal logic.

- a) $F(A,B,C,D) = \sum m(1,5,6,12,13,14) + d(2,4)$ (05)
- b) $F(A,B,C,D) = \pi M(0,1,2,3,4,7)$ (05)

OR

Q.2 State and prove De Morgan's Theorems. Reduce the expression $\sum m(0,2,3,4,5,6)$ using mapping and implement in NAND logic. (10)

Q.3 State rules for BCD addition. Design BCD adder using two 4-bit Binary adders. (10)

OR

Q.3 Design following 4-bit code converters with the help of truth table and k-map simplification. (10)

- a) Binary to Gray code converter
- b) Gray to Binary code converter

Q.4 Describe working of T-flip flop and SR-flip flop with the help of truth table. (10)

OR

Q.4 Differentiate Asynchronous counters and Synchronous counters. Design 2-bit asynchronous counter using flip flops with the help of timing diagram. (10)

Q.5 Develop an ASM chart and draw state diagram to detect the sequence 1010. (10)

OR

Q.5 Explain the following state machines in detail : (10)

- a) Moore state machine
- b) Mealy state machine

Q.6 Write a short note on : Programmable Logic Devices, Explain any one PLD in detail. (10)

OR

Q.6 Give the logic implementation of (10)

- a) 32 x 4-bit ROM using a decoder of suitable size.
- b) 8 x 4-bit ROM using a decoder of suitable size.

* * * * *