

BACHELOR OF TECHNOLOGY (CBCS) (2021-COURSE)
B. Tech. Sem - II COMPUTER SCIENCE & BUSINESS SYSTEMS : SUMMER : 2024
SUBJECT: PRINCIPLES OF ELECTRONICS ENGINEERING

Day : Monday
Date : 03/06/2024

S-24140-2024

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labelled diagram **WHEREVER** necessary.
- 4) Use of non – programmable **CALCULATOR** is allowed.
- 5) Assume suitable data if necessary.

Q.1 Draw and explain the effect of increase in temperature on Intrinsic semiconductor with suitable diagram. Draw covalent bonding structure of the same. (10)

OR

Q.1 Sketch energy band diagram of P and N type extrinsic semiconductor also explain fermi energy levels for the same types. (10)

Q.2 Describe the forward and reverse biasing of P-N junction diode. Draw the characteristics graph and define knee voltage and breakdown voltage. (10)

OR

Q.2 Draw and explain working of full wave rectifier with center –tap transformer. Define ripple factor and efficiency for the same. (10)

Q.3 What is Transistor? Explain the operation of NPN transistor in active region with suitable diagram and show the flow of charge carriers. What is meant by majority and minority carriers? (10)

OR

Q.3 Draw and explain input and output characteristics of Common Emitter configuration for NPN transistor. Describe β of CE configuration. (10)

Q.4 Draw and explain common source and common gate configurations used in JFET amplifier. (10)

OR

Q.4 Draw and explain the construction and working of N–channel depletion type MOSFET. Also draw drain and transfer characteristic graph. (10)

Q.5 Explain types of feedbacks in amplifiers. Describe Barkhausen criteria for oscillation in detail. (10)

OR

Q.5 Draw and explain the operational amplifier in Inverting and Non–Inverting mode. (10)

Q.6 Draw and explain full adder and full subtractor with logic diagram and truth table. (10)

OR

Q.6 What is shift register? Draw and explain operation of 4 –bit serial–in parallel out (SIPO- right shift) shift register. (10)

* * *