

B.Tech. SEM -V (E & TC Engg.) 2014 Course (CBCS) : WINTER - 2018
SUBJECT: POWER DEVICES AND MACHINES

Day : Thursday
Date : 29/11/2018

W-2018-2438

Time: 02.30 PM TO 05.30 PM
Max. Marks: 60

N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labeled diagram **WHEREVER** necessary.
- 4) Assume suitable data, if necessary.

Q. 1 Explain power MOSFET with respect to construction, operation and characteristics. (10)

OR

Explain power BJT with its structure and switching characteristics. (10)

Q. 2 Explain two transistor analogy of SCR with its triggering and isolation techniques. (10)

OR

Explain GTO with its applications. (10)

Q. 3 Write down the effects of freewheeling diode with output waveform for single phase converter. (10)

OR

Explain three phase full converter with neat circuit diagram and operational waveforms. (10)

Q. 4 Write down working principles of single phase bridge inverter for R and RL load. (10)

OR

How PWM technique is used for harmonic reduction in inverter? (10)

Q. 5 Write a note on 'Induction Motor'. (10)

OR

Explain DC motor with its working principles, construction and applications. (10)

Q. 6 Explain illumination and lightning control protocols. (10)

OR

Write a note on: (10)

- a) Solar PV
- b) LED Drives

* * * * *