

BACHELOR OF TECHNOLOGY (CBCS - 2023)
B. Tech. Sem-II Computer Science & Business Systems : SUMMER : 2025
SUBJECT: DATA STRUCTURES & ALGORITHMS

Day : Wednesday
Date : 28/05/2025

S-27709-2025

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of non-programmable calculator is allowed.
- 4) Assume suitable data if necessary.

Q.1 Define algorithm. Discuss the key characteristics of algorithms. (10)

OR

Define recurrence relation. Discuss substitution technique with example.

Q.2 Define linked list. Write the basic operations that can be performed on linked list. (10)

OR

Differentiate between stack and queue.

Q.3 Define B tree. Discuss that various cases of deletion of element from the B Tree with example. (10)

OR

Create a B+ tree of the Order 4 for the given elements 1, 4, 7, 10, 17, 21, 31, 25, 19, 20, 28, 42.

Q.4 Define Minimum Spanning tree and discuss Minimum Spanning tree algorithms. (10)

OR

Discuss directed and undirected graph with examples.

Q.5 Discuss quick sort algorithm and sort the following elements using quick sort. (10, 80, 30, 90, 40, 50, 70) (10)

OR

What is a Heap? Discuss working of heap sort algorithm examples with time complexity.

Q.6 Explain the concept of hashing and how it can be used for fast key-based access in hashed file organization. (10)

OR

Discuss the challenges and limitations of existing file organization methods?

* * * *

BACHELOR OF TECHNOLOGY (CBCS - 2023)
B. Tech. Sem-II Computer Science & Business Systems : SUMMER : 2025
SUBJECT: PRINCIPLES OF ELECTRONICS ENGINEERING

Day : Friday
Date : 30/05/2025

S-27710-2025

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat diagrams **WHEREVER** necessary.
- 4) Assume suitable data, if necessary.

Q. 1 Explain conductor, semiconductor and insulator with the help of Energy band diagram. (10)

OR

Q. 1 Describe the drift current and diffusion current with the help of diagram in detail. (10)

Q.2 With a neat sketch explain the working of (10)
i) Centre – tap full – wave rectifier ii) full – wave bridge rectifier

OR

Q. 2 Sketch the V – I characteristics of P – N junction diode. Describe Zener breakdown and Avalanche Breakdown in detail. (10)

Q. 3 Define the current amplification factor for common emitter configuration, common base configuration, and common collector configuration. Derive the relation between them. (10)

OR

Q. 3 Describe the need of biasing circuits in Transistor. Explain the operation of fixed bias circuit with input and output equations and state advantages and disadvantages of same circuit. (10)

Q. 4 Draw and explain operation of n – channel depletion type MOSFET with Drain and Transfer characteristic graph. (10)

OR

Q. 4 Explain common source and common gate configuration of MOSFET with circuit diagram (10)

Q. 5 Explain the inverting and non – inverting mode of operation. Write a short note on voltage follower in Op – Amp. (10)

OR

Q. 5 What is meant by feedback? Explain Inverting and Non – Inverting amplifier with diagram. (10)

Q. 6 i) Reduce the expression using K – map. (10)
 $F(A,B,C,D) = \sum m(0,1,3,4,5,6,7,13,15)$
ii) Explain Half adder and Half subtractor.

OR

Q. 6 Which gates are called universal gates and why? Explain DeMorgans first and second theorem with truth table and logic diagram. (10)

* * * * *