

BACHELOR OF TECHNOLOGY (C.B.C.S.) (2021-COURSE)
B. Tech. Sem - I Computer Science & Business System : WINTER- 2022
SUBJECT : PRINCIPLES OF ELECTRICAL ENGINEERING

Day : Friday

Time : 10:00 AM-01:00 PM

Date : 13-01-2023

W-24132-2022

Max. Marks : 60

N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labelled diagrams **WHEREVER** necessary.
- 4) Use of non-programmable calculator is **ALLOWED**.
- 5) Assume suitable data, if necessary.

Q. 1 Define and write down the units of : (10)

- | | |
|---------------------------|----------------|
| i) EMF | iv) Resistance |
| ii) Current | v) Work |
| iii) Potential Difference | |


OR

- a) An electric kettle supplied from 230 V D.C. supply is required to heat 1 kg of water from 40° C to boiling point in 10 minutes. If the efficiency of the kettle is 80 %, calculate the resistance of the heating element of the kettle. The specific heat of water is 4180 J/kg. (05)
- b) State and explain Kirchoff's current and voltage law. (05)

Q. 2 State and explain maximum power transfer theorem. Derive the condition for maximum power transfer in resistive circuit. (10)

OR

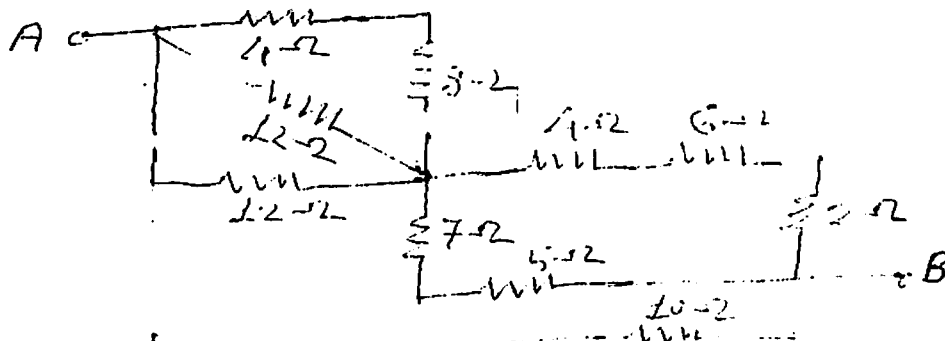- a) Derive the equations to convert delta connected resistive network into equivalent star connected network. (06)
- b) Calculate net resistance between terminals A and B. (04)



Q. 3 a) Draw and explain power triangle in detail. (05)

b) A series R-L circuit with $R = 50 \Omega$ and $L = 0.2 \text{ H}$ is connected to 250 V, 50 Hz source. Calculate: (05)

- i) Impedance
- ii) Current
- iii) Power factor
- iv) Active power
- v) Draw vector diagram

P. T. O.

OR

- a) Sketch A.C. waveform and define the following terms related to A.C. circuit: (05)
- | | |
|-----------------|----------------|
| i) Form factor | iii) Impedance |
| ii) Peak factor | iv) Admittance |
- b) Explain the concept of resonance in series R-L-C circuit in short. (05)

- Q. 4 a) Define the following terms: (05)
- | | |
|-----------------------------|---------------------------|
| i) Electrostatic field | iv) Electric flux density |
| ii) Electric field strength | v) Permittivity |
| iii) Electric flux | |

- b) Three capacitors of values $4\mu F$, $8\mu F$ and $12\mu F$ value have an applied voltage of 120 V across their series combination. Determine the voltage on each of the capacitors. (05)

OR

Define battery and list out its different types. Explain construction and working of lead-acid battery in detail and also discuss different applications of lead-acid battery. (10)

- Q. 5 a) State and explain Faraday's law of electromagnetic induction. (05)
- b) Define transformer and explain different types of losses in single phase transformer. (05)

OR

- a) Compare magnetic circuit and electric circuit. (05)
- b) Discuss B-H curve for magnetic material in short. (05)

- Q. 6 a) Sketch and explain basic layout of distribution system. (05)
- b) Define earthing and discuss the importance of earthing in electrical system. (05)

OR

List out different types of wiring system. Explain cleat wiring in detail along with its advantages, limitations and applications. (10)

* * * * *