

BACHELOR OF TECHNOLOGY (CBCS - 2023)
B. Tech. Sem-II Computer Science & Business Systems : WINTER: 2025
SUBJECT: PRINCIPLES OF ELECTRONICS ENGINEERING

Day : Friday
Date : 28/11/2025

W-27710-2025

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat diagrams **WHEREVER** necessary.
- 4) Assume suitable data, if necessary.

Q. 1 Describe the valence band, conduction band and forbidden energy gap with the help of energy level diagram. (10)

OR

Q. 1 Draw and explain P – type and N – type Extrinsic semiconductors in detail with diagram. Also define majority and minority carriers in both types of extrinsic semiconductors. (10)

Q.2 Explain forward and reverse biasing of P – N junction diode with the help of circuit diagram and waveforms. Also show knee voltage for Silicon and Germanium diode on characteristic graph. (10)

OR

Q. 2 What is mean by DC load line and explain Quiescent (Q) Point. Draw and explain linear Piecewise model for diode. (10)

Q. 3 Write short notes on the following: (10)
i) Advantages of transistor ii) Operating point iii) d.c. load line

OR

Q. 3 Define the current amplification factor for common emitter configuration, common base configuration and common collector configuration. Derive the relation between them. (10)

Q. 4 Explain the working principle of CMOS in detail. Give the advantages and disadvantages of CMOS. (10)

OR

Q. 4 Describe the construction and operation of N – channel JFET in detail. Also draw the drain characteristics and transfer characteristics graph. (10)

Q. 5 Draw and explain the operation of Op-Amp as Integrator and differentiator in detail. (10)

OR

Q. 5 Describe the effect of positive feedback in amplifier circuit. Explain Barkhausen criteria for oscillation. (10)

Q. 6 Explain in detail the following flip – flops with their truth table. (10)
i) S-R flip flop ii) D flip flop iii) J-K flip – flop iv) T flip – flop

OR

Q. 6 i) Describe the operation of S-R clocked flip – flop with the help of Truth table (10)
ii) Describe 1:2 De – multiplexer with suitable diagram.

* * * * *