

BACHELOR OF TECHNOLOGY (C.B.C.S.) (2020 COURSE)
B.Tech.Sem - IV Electronic & Communication : WINTER- 2022
SUBJECT : INTEGRATED CIRCUITS & AMPLIFIER DESIGN

Day : Tuesday

Time : 02:30 PM-05:30 PM

Date : 29-11-2022

W-24604-2022

Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Use of non-programmable calculator is **allowed**.
- 4) Assume suitable data **WHEREVER** necessary.
- 5) Draw neat diagram **WHEREVER** necessary.

- Q.1 a) What is the need of level shifter block in op-amp? Draw any three circuits of level shifter and derive the expression for it. (07)
b) What are the three operating temperature ranges of the IC? (03)

OR

- Q.1 a) Define input offset voltage for an op-amp. Also discuss internal and external offset voltage compensation techniques in detail. (07)
b) Compare digital and linear IC's. (03)

- Q.2 a) Design a differentiator using op-amp to differentiate an input signal that varies in frequency from 10Hz to about 10KHz. (07)
b) Describe with the help of circuit diagram I to V converter. (03)

OR

- Q.2 Describe in detail with the help of circuit diagrams and waveforms the positive clipper and negative clipper. (10)

- Q.3 a) Discuss the operation of full wave precision rectifier with neat circuit diagram and waveforms. (07)
b) What is the difference between a basic comparator and the Schmitt trigger? (03)

OR

- Q.3 a) Describe any three performance parameters of sample and hold circuit. (06)
b) Draw the circuit diagram of log amplifier using op-amp and derive its output equation. (04)

- Q.4 a) Draw the circuit diagram for band pass filter and discuss its operation with the help of frequency response. (07)
b) What are the advantages of active filters over passive filters? (03)

OR

- Q.4 Design a sawtooth waveform generator using op-amp IC741 for $f_0=1\text{KHz}$ and $V_0=4\text{Vp-p}$ (10)

- Q.5 With the help of neat block diagram discuss the principle of operation of phase locked loop. Describe any one application of PLL in detail. (10)

OR

- Q.5 Design an IC555 based square wave generator to produce a symmetrical square wave of 2KHz, if $V_{cc} = 12\text{V}$. Draw the voltage waveform across timing capacitor and the output. (10)

- Q.6 Derive the output voltage expression for a 3 bit R-2R ladder type D to A converter using op-amp. (10)

OR

- Q.6 a) Which are the different techniques used to convert analog signal into the digital signal. Discuss merits and demerits of each technique. (07)
b) Differentiate between A to D converter and D to A converter. (03)
